



VI Semester B.E. (E & E) Degree Examination, June/July 2017
(2K11 Scheme)

EE602 : POWER SYSTEM ANALYSIS

Time : 3 Hours

Max. Marks : 100

Instruction : Answer **any 5 full** questions choosing at least **2** from **each** Part.

PART – A

1. a) What is per unit quantity ? Enumerate the advantages of per unit quantity. **5**
b) Show that the p.u. impedance of a transformer is same on both primary and secondary sides. **5**
c) The figure 1 (c) shows the diagram of a radial transmission system. A load of 60 MW at 0.9 p.f. Lag is tapped at 60 KV as shown. Determine the terminal voltage of the generator at bus 1. The ratings of transformers are
 $T_1 = 3 \text{ phase, } 50 \text{ Hz, } 100 \text{ MVA, } 11 \text{ K V Y} - 220 \text{ KV } \Delta, X = 10 \%$
 $T_2 = 3 \text{ phase, } 50 \text{ Hz, } 80 \text{ MVA, } 220 \text{ KV } \Delta - 66 \text{ KV Y, } X = 10 \%$ **10**

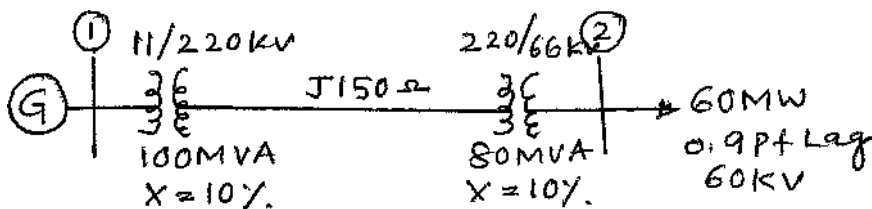


Fig. 1 (c)

2. a) Explain clearly the variation of current and impedance of an alternator when a 3 phase sudden short circuit occurs at its terminals. **10**
b) A synchronous generator and motor are rated for 30000 KVA, 13.2 KV and both have subtransient reactance of 20 %. The line connecting them has a reactance of 10 % on the base of machine ratings. The motor is drawing 20000 KW at 0.8 p.f. leading. The terminal voltage of the motor is 12.8 KV. When a symmetrical three phase fault occurs at motor terminals. Find the subtransient current in generator, motor and at the fault point. **10**



3. a) Obtain an expression for the three phase complex power in terms of symmetrical components. **10**
- b) A delta connected resistive load is connected across a balanced supply of 400 V as shown in figure 3 (b). Find the symmetrical components of line currents and delta currents. **10**

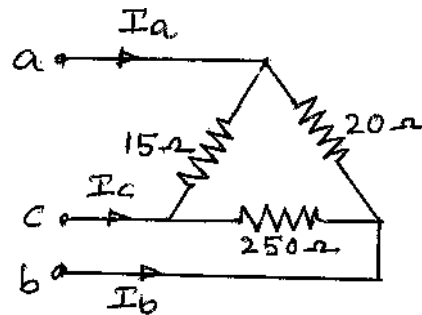


Fig. 3 (b)

4. a) Prove that in symmetrical system, currents of a given sequence produce voltage drops of the same sequence only. 10
- b) Draw the positive, negative and zero sequence networks for the power system shown in figure 4 (b) choose a base of 50 MVA, 220 KV in the 50 Ω transmission lines and mark all the reactances in p.u. The ratings of the generators and transformers are
- Generator 1 : 25 MVA, 11 KV, $X'' = 20\%$
- Generator 2 : 25 MVA, 11 KV, $X'' = 20\%$
- Three phase transformer (each) = 20 MVA 11 Y/220 Y KV, $X = 15\%$.
- The negative sequence reactance of each synchronous machine is equal to the subtransient reactance. The zero sequence reactance of each machine is 8 %. Assume that the zero sequence reactances of each lines are 250 % of their positive sequence reactances. 10

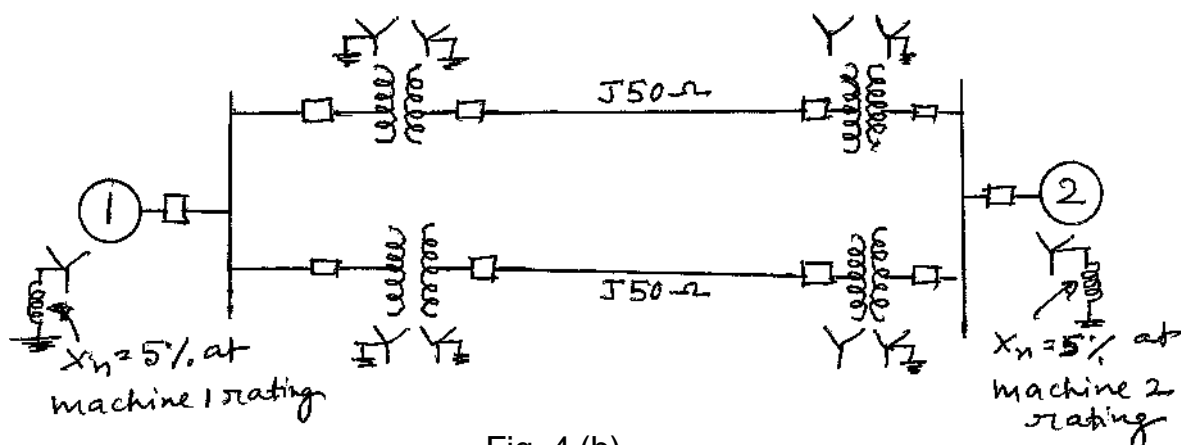


Fig. 4 (b)



PART – B

5. a) A single line to ground fault occurs at the terminals of an unloaded generator through a fault impedance Z_F . Assume that the neutral of the is grounded through a reactance Z_n . Derive the expression for fault current. Draw the connection of sequence networks to represent the fault. **10**
- b) A three phase generator with line to line voltages of 400 V is subjected to double line to ground fault. If $Z_1 = j 2 \Omega$, $Z_2 = j 0.5 \Omega$ and $Z_0 = j 0.25 \Omega$. Determine the fault current and terminal voltages. **10**
6. a) For i) one conductor open fault and
ii) two conductor open fault
Obtain expressions for currents and show the connections of sequence networks to represent the faults. **8**
- b) A synchronous motor is receiving 10 MW of power at 0.8 pf lag at 6 KV. Double line to ground fault takes place at the middle point of the transmission line as shown in figure 6 (b). Find the fault current.
The ratings of the generator, motor and transformer are as follows.
Generator : 20 MVA, 11 KV, $X_1 = 0.2 \text{ PU}$, $X_2 = 0.1 \text{ PU}$, $X_0 = 0.1 \text{ PU}$
Transformer T_1 : 18 MVA, 11.5 Y/34.5 KV, $X = 0.1 \text{ PU}$
Transmission line : $X_1 = X_2 = 5 \Omega$, $X_0 = 10 \Omega$
Transformer T_2 : 15 MVA, 6.9 Y – 34.5 Y KV, $X = 0.1 \text{ PU}$
Motor : 15 MVA, 6.9 KV, $X_1 = 0.2 \text{ PU}$, $X_2 = X_0 = 0.1 \text{ PU}$
Consider the base values of 20 MVA, 11 KV on the generator side. **12**

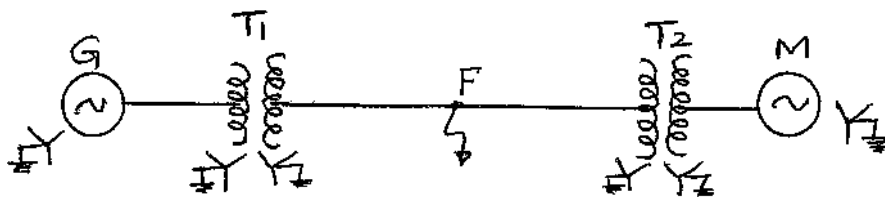


Fig. 6 (b)



7. a) Derive swing equation for a synchronous machine. **10**
- b) A turbogenerator 6 pole, 50 Hz of capacity 80 MW working at 0.8 pf has an inertia of 10 MJ/MVA.
- i) Calculate the energy stored in the rotor at synchronous speed
 - ii) Find rotor acceleration if the mechanical input is suddenly raised to 75 MW for an electrical load of 60 MW.
 - iii) Suppose the above acceleration is maintained for a duration of 6 cycles, calculate the change in torque angle and rotor speed at the end of 6 cycles. **10**
8. a) Explain the complete block diagram representation of load frequency control of an isolated power system. **12**
- b) Two generators rated 200 MW and 400 MW are operating in parallel. The droop characteristics of their governors are 4 % and 5 % respectively from no load to full load. Assuming that the generators are operating at 50 Hz at no load, how would a load of 600 MW be shared between them ? What will be the system frequency at this load ? Assume free governor operation. **8**
-